

Memory Interfacing

After Mid

Chip Identification:

→ 2 memory element: EPROM, RAM

1) EPROM: IC - 27 XXX, IC 27 XX

2) RAM: IC 61/62 XXX

EX-1:

IC 27 512

1st two digit memory type

Size of memory

Type

in Kbits.

→ Memory Size = 512 Kbits = $\frac{512}{8}$ KB = 64 KB

→ That's memory is EPROM 64 KB memory.

EX-2

IC 62 64


1st two digit is memory type

Size of memory in Kbits.

→ Memory Size = 64 Kbits = $\frac{64}{8}$ KB = 8 KB

→ That's memory is RAM 8 KB memory.

Memory Organization:

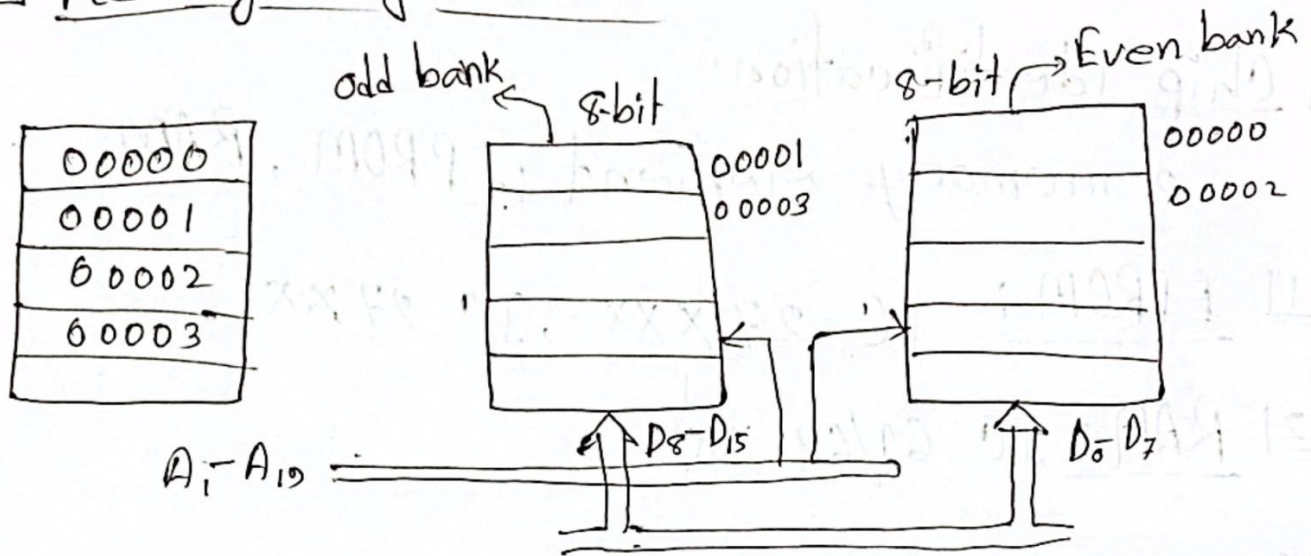

- => Absolute / Full decoding chip selector
এই সবসময় bit নিম্নে কাজ করতে হবে।
- => Partial decoder decoding chip selector
এই 2/3 টি bit নিম্নে কাজ করতে হবে।
- => Memory ৩ টি থাকলে আমরা বিজোড় সংখ্যক memory থাকলে 2 টি একসাথে কাজ করতে হবে
অর্থাৎ pair করে করতে হবে।
- => If Memory Size same না এবং Memory Size same হলেও। আমরা Memory Size same কিন্তু memory same নাহলে pair করা
পারবে না। ~~এই~~ Same memory and same size হলে 2 টি memory pair করে কাজ
করতে পারবে।

P-1: Interface two 4K x 8 EPROM and 4K x 8 RAM chip with 8086.

Solⁿ: Given that,

Memory size of

$$\text{EPROM} = 4K \times 8 = 2^2 \cdot 2^{10} \times 8 = 2^{12} \times 8$$

$$\text{RAM} = 4K \times 8 = 2^2 \cdot 2^{10} \times 8 = 2^{12} \times 8$$

$\therefore$ Address line = 12


	A ₁₉	A ₁₈	A ₁₇	A ₁₆	A ₁₅	A ₁₄	A ₁₃	A ₁₂	A ₁₁	...	A ₁	A ₀
EPROM-I	0	0	0	0	0	0	0	0	0	...	0	0
	0	0	0	0	0	0	0	1	1	...	1	0

EPROM-II	0	0	0	0	0	0	0	0	0	...	0	1
	0	0	0	0	0	0	0	1	1	...	1	1

RAM-I	0	0	0	0	0	0	0	0	0	...	0	0
	1	0	0	0	0	0	0	1	1	...	1	0

RAM-II	1	0	0	0	0	0	0	0	0	...	0	1
	1	0	0	0	0	0	0	1	1	...	1	1

Diagram;

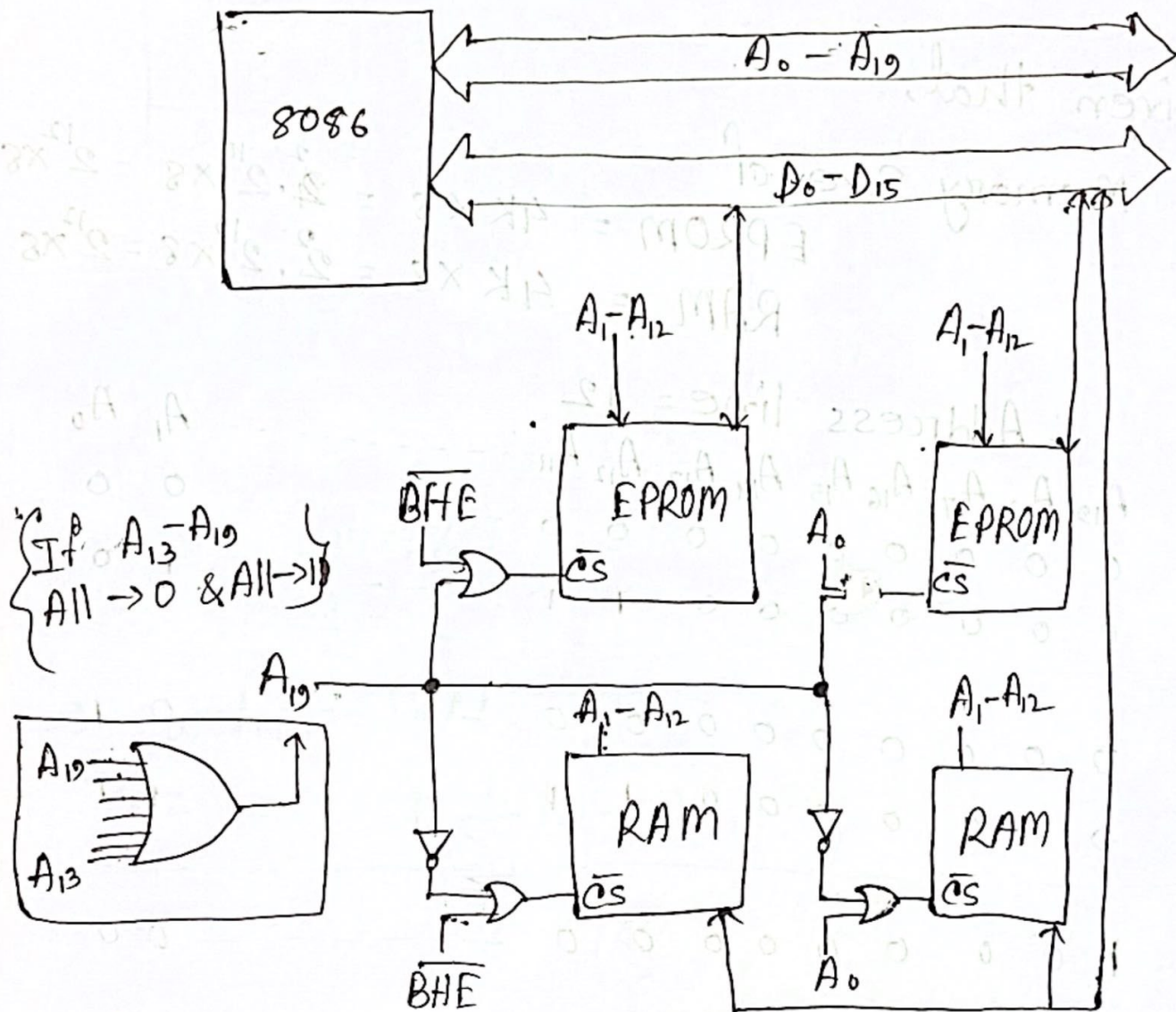

P-2: Interface 32KB of RAM memory to the 8086 microprocessor system using absolute decoding with the suitable address.

Solⁿ:

Given that,

Total RAM = 32 KB


$\therefore$ Even and odd Bank = $\frac{32}{2}$ KB = 16 KB

$$= 2^4 \cdot 2^{10} \times 8 = 2^{14} \times 8$$

$\therefore$ Address Line = 14

	A_{19}	A_{18}	A_{17}	A_{16}	A_{15}	A_{14}	A_{13}	-----	A_1	A_0
RAM-I	0	0	0	0	0	0	0	-----	0	0
	0	0	0	0	0	1	1	-----	1	0
RAM-II	0	0	0	0	0	0	0	-----	0	1
	0	0	0	0	0	1	1	-----	1	1

Diagram

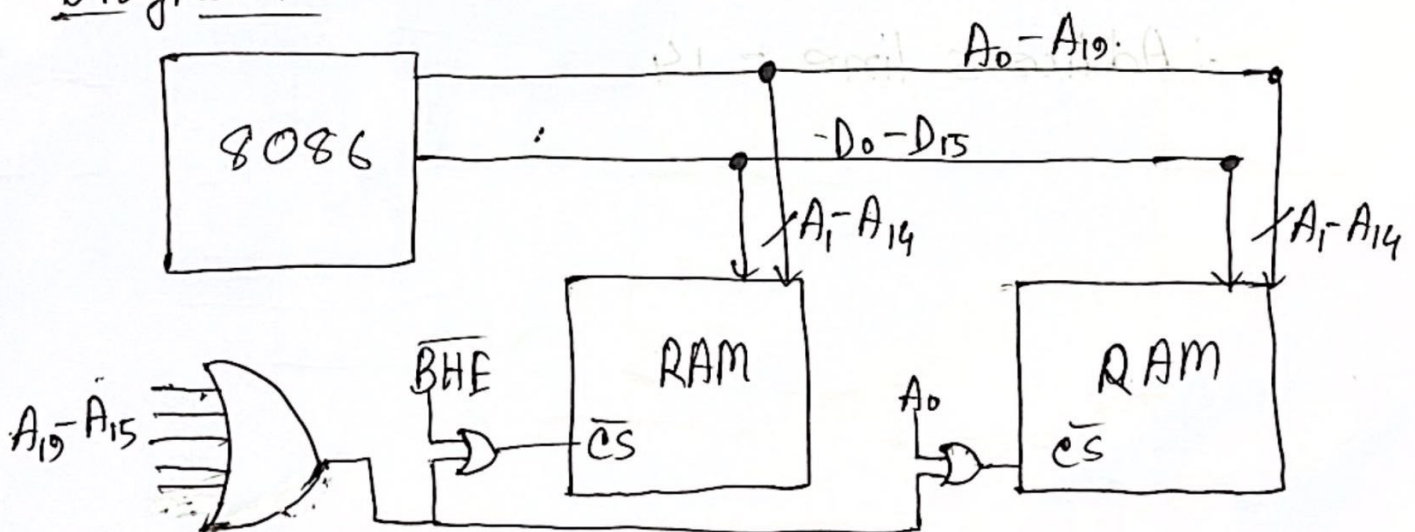

P-3: Interface 32K word of memory to the 8086 microprocessor system. Available memory chips are 16K x 8 RAM use suitable decoder for generating chip select logic.

Solⁿ:

we know that,

$$\text{word} = 16 \text{ bits} = 2 \text{ B}$$

Required memory

$$32 \text{ K words} = 32 \text{ K} \times 2 \text{ B}$$


$$= 64 \text{ KB}$$

$$\therefore \text{Each RAM chip} = 16 \text{ K} \times 8 = 16 \text{ KB}$$

$$\therefore \text{So, number of chips required} = \frac{64 \text{ KB}}{16 \text{ KB}} = 4 \text{ chips}$$


$$\text{RAM} \rightarrow 16 \text{ KB} = 2^4 \cdot 2^{10} \times 8 = 2^{14} \times 8$$

$$\therefore \text{Address line} = 14$$

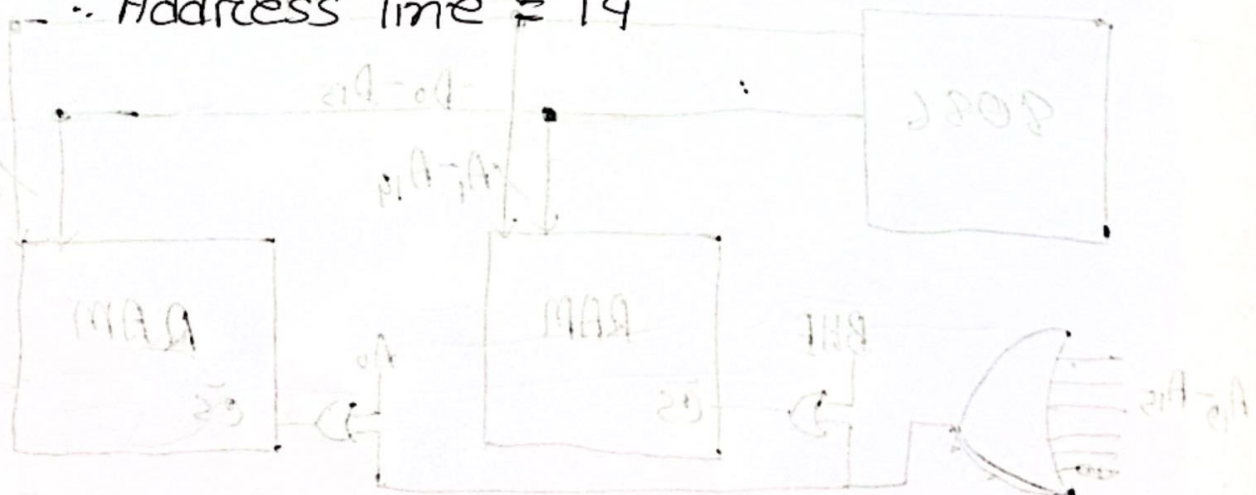

	A_{19}	A_{18}	A_{17}	A_{16}	A_{15}	A_{14}	A_{13}	...	A_1	A_0
RAM-I	0	0	0	0	0	0	0	...	0	0
	0	0	0	0	0	1	1	...	1	0
RAM-II	0	0	0	0	0	0	0	...	0	1
	0	0	0	0	0	1	1	...	1	1
RAM-III	1	0	0	0	0	0	0	...	0	0
	1	0	0	0	0	1	1	...	1	1
RAM-IV	1	0	0	0	0	0	0	...	0	1
	1	0	0	0	0	1	1	...	1	1

Diagram:

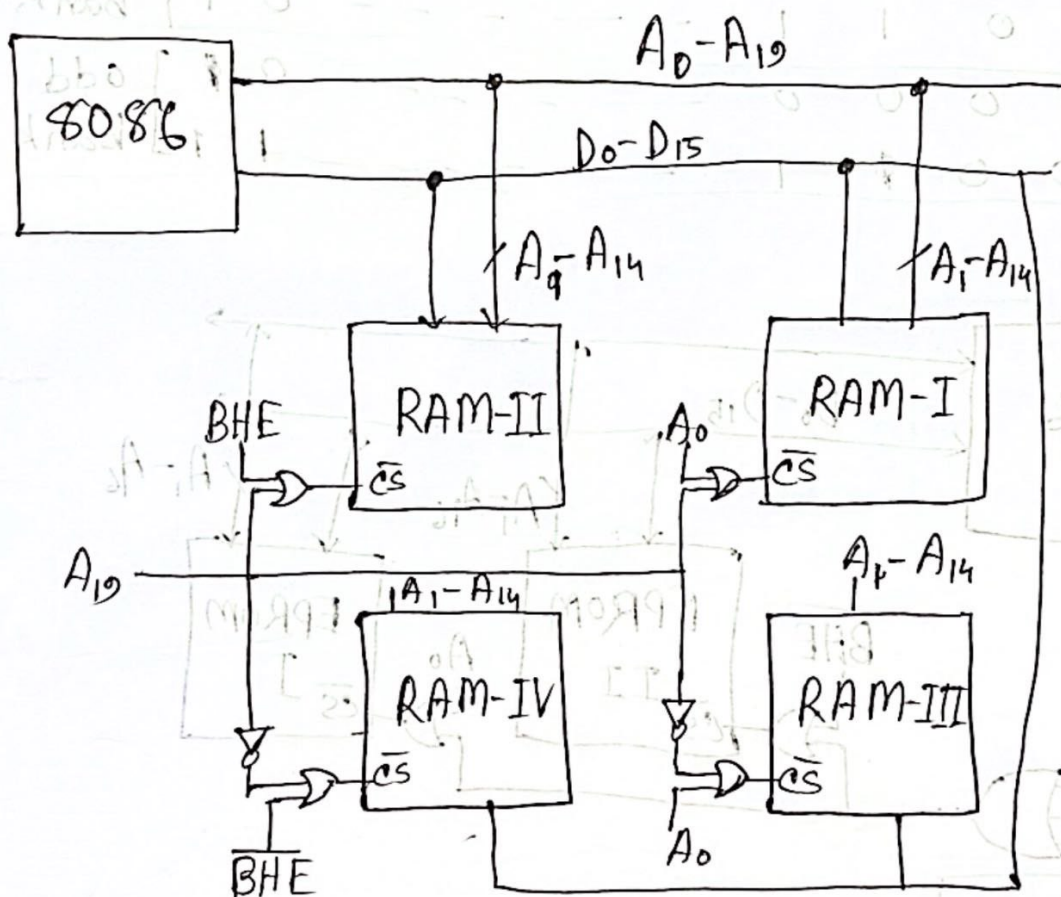

P-4: Interface microprocessor 8086 with two number of IC-27512 chip.

Solⁿ:

Given that,

2 number of IC-27512 $\rightarrow$ EPROM

$$\therefore \text{memory size} = \frac{512}{8} \text{ KB} = 64 \text{ KB}$$

$$= 2^6 \times 8$$

$$\therefore \text{Address line} = 16$$

$$= 2^{16} \times 8$$

	A_{19}	A_{18}	A_{17}	A_{16}	A_{15}	...	A_1	A_0	
EPROM - I	0	0	0	0	0	...	0	0	Even bank
	0	0	0	1	1	...	0	1	
EPROM - II	0	0	0	0	0	...	0	0	odd bank
	0	0	0	1	1	...	1	1	

Diagram

