

Memory Interfacing

After Mid

Chip Identification:

→ 2 memory element: EPROM, RAM

1) EPROM: IC - 27 XXX, IC 27 XX

2) RAM: IC 61/62 XXX

EX-1:

IC 27 512

1st two digit memory
Type

Size of memory
in Kbits.

→ Memory Size = 512 Kbits = $\frac{512}{8}$ KB = 64 KB

→ That's memory is EPROM 64 KB memory.

EX-2

IC 62 64


1st two digit is
memory type

Size of memory
in Kbits.

→ Memory Size = 64 Kbits = $\frac{64}{8}$ KB = 8 KB

→ That's memory is RAM 8 KB memory.

Memory Organization:

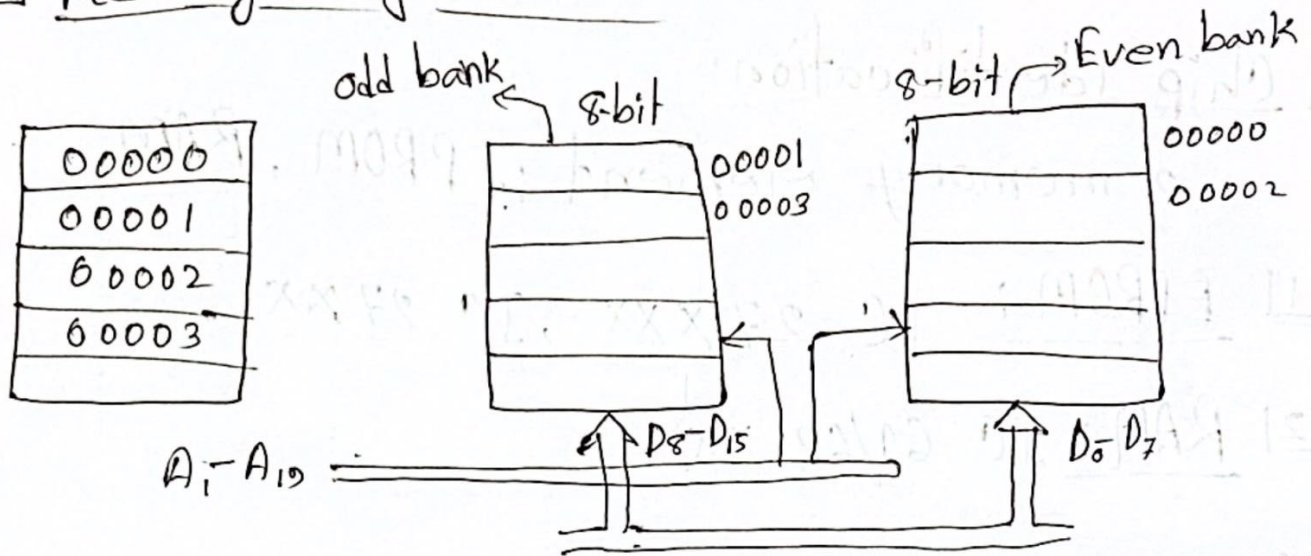

- => Absolute / Full decoding chip selector
এই সবসময় bit নিম্ন কাজ করতে হবে।
- => Partial decoder decoding chip selector
এই 2/3 টি bit নিম্ন কাজ করতে হবে।
- => Memory ৩ টি থাকলে অথবা বিজোড় সংখ্যক memory থাকলে 2 টি একসাথে কাজ করতে হবে অথবা pair করে করতে হবে।
- => If Memory Size same না এবং Memory Size same হলেও। অথবা Memory Size same কিন্তু memory same নাহলে pair করা পারবে না। ~~এই~~ Same memory and same size হলে 2 টি memory pair করে কাজ করতে পারবে।

P-1: Interface two 4K x 8 EPROM and 4K x 8 RAM chip with 8086.

Solⁿ: Given that,

Memory size of


$$\text{EPROM} = 4K \times 8 = 2^2 \cdot 2^{10} \times 8 = 2^{12} \times 8$$

$$\text{RAM} = 4K \times 8 = 2^2 \cdot 2^{10} \times 8 = 2^{12} \times 8$$

$\therefore$ Address line = 12

	A_{19}	A_{18}	A_{17}	A_{16}	A_{15}	A_{14}	A_{13}	A_{12}	A_{11}	...	A_1	A_0
EPROM-I	0	0	0	0	0	0	0	0	0	...	0	0
	0	0	0	0	0	0	0	1	1	...	1	0
EPROM-II	0	0	0	0	0	0	0	0	0	...	0	1
	0	0	0	0	0	0	0	1	1	...	1	1
RAM-I	0	0	0	0	0	0	0	0	0	...	0	0
	1	0	0	0	0	0	0	1	1	...	1	0
RAM-II	1	0	0	0	0	0	0	0	0	...	0	1
	1	0	0	0	0	0	0	1	1	...	1	1

Diagram;

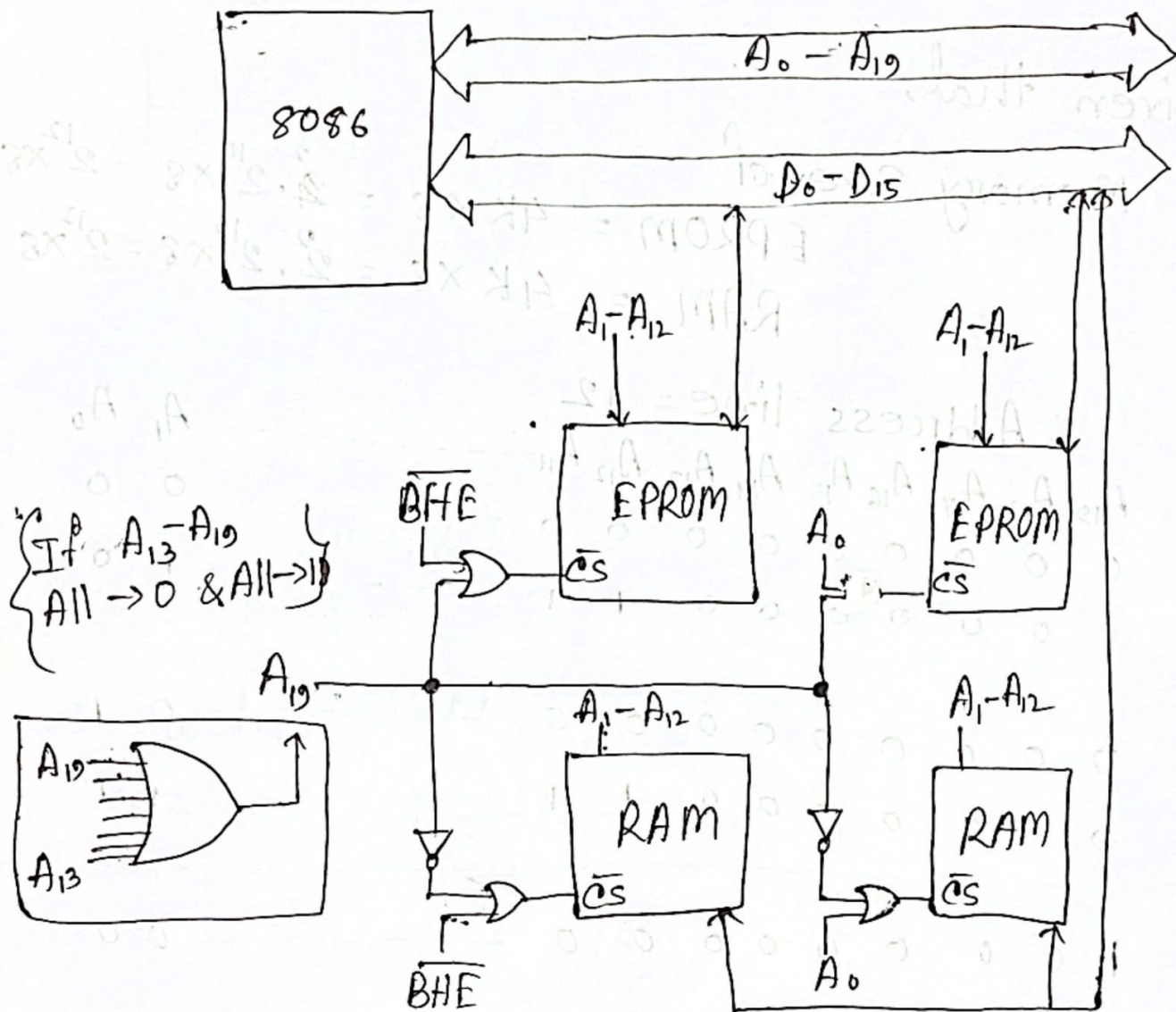

P-2: Interface 32KB of RAM memory to the 8086 microprocessor system using absolute decoding with suitable address.

Solⁿ:

Given that,

Total RAM = 32 KB


$\therefore$ Even and odd Bank = $\frac{32}{2}$ KB = 16 KB

$$= 2^4 \cdot 2^{10} \times 8 = 2^{14} \times 8$$

$\therefore$ Address Line = 14

	A_{19}	A_{18}	A_{17}	A_{16}	A_{15}	A_{14}	A_{13}	-----	A_1	A_0
RAM-I	0	0	0	0	0	0	0	-----	0	0
	0	0	0	0	0	1	1	-----	1	0
RAM-II	0	0	0	0	0	0	0	-----	0	1
	0	0	0	0	0	1	1	-----	1	1

Diagram

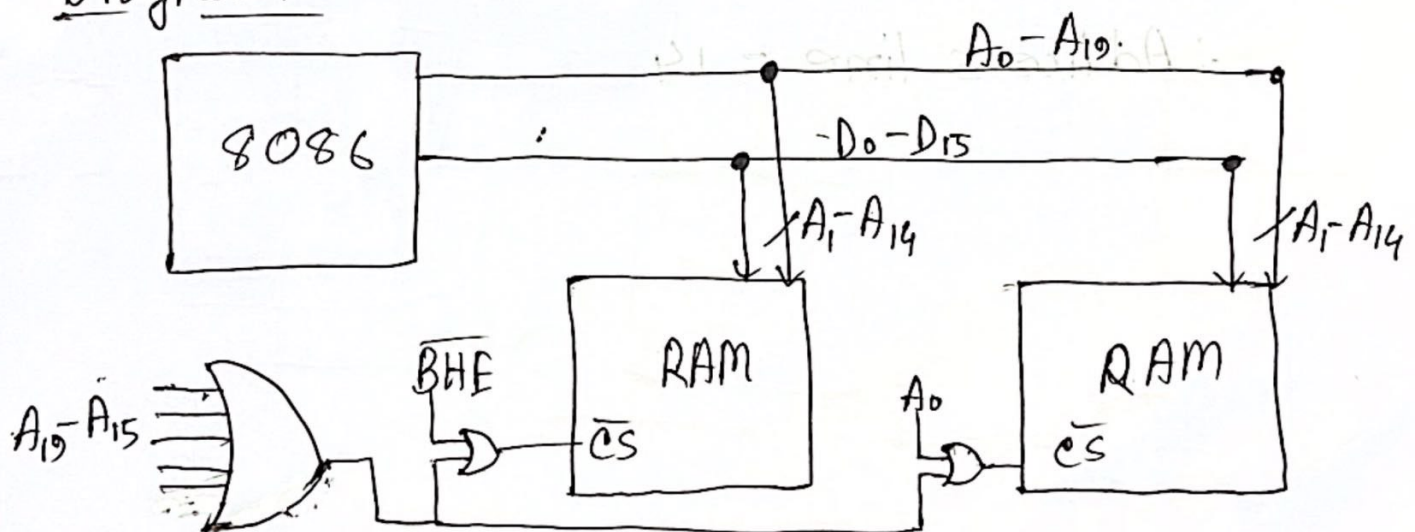

P-3: Interface 32K word of memory to the 8086 microprocessor system. Available memory chips are 16K x 8 RAM use suitable decoder for generating chip select logic.

Solⁿ:

we know that,

$$\text{word} = 16 \text{ bits} = 2 \text{ B}$$

Required memory

$$32 \text{ K words} = 32 \text{ K} \times 2 \text{ B}$$


$$= 64 \text{ KB}$$

$$\therefore \text{Each RAM chip} = 16 \text{ K} \times 8 = 16 \text{ KB}$$

$$\therefore \text{So, number of chips required} = \frac{64 \text{ KB}}{16 \text{ KB}} = 4 \text{ chips}$$


$$\text{RAM} \rightarrow 16 \text{ KB} = 2^4 \cdot 2^{10} \times 8 = 2^{14} \times 8$$

$$\therefore \text{Address line} = 14$$

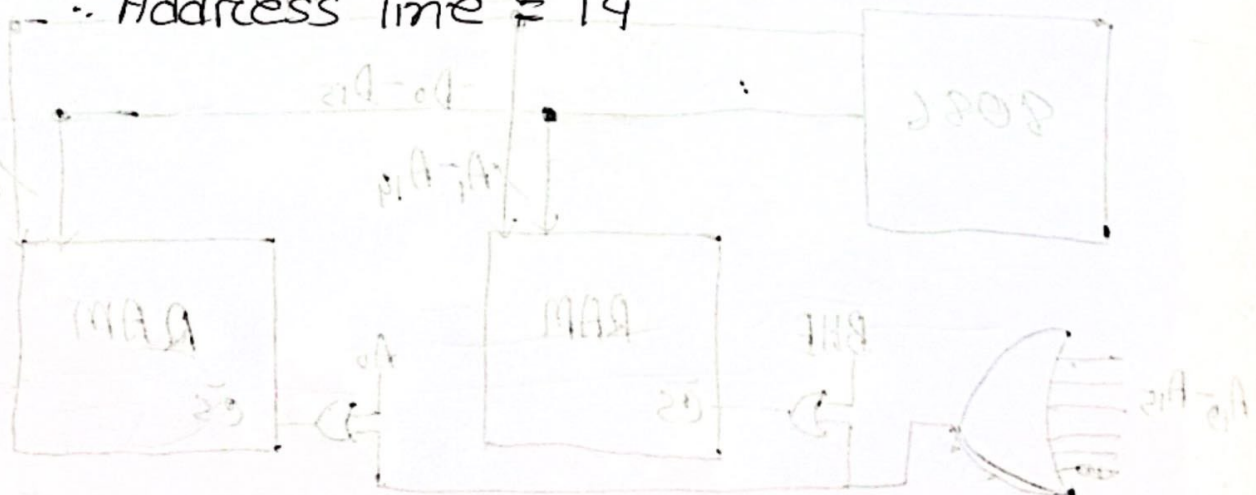

	A_{19}	A_{18}	A_{17}	A_{16}	A_{15}	A_{14}	A_{13}	...	A_1	A_0
RAM-I	0	0	0	0	0	0	0	...	0	0
	0	0	0	0	0	1	1	...	1	0
RAM-II	0	0	0	0	0	0	0	...	0	1
	0	0	0	0	0	1	1	...	1	1
RAM-III	1	0	0	0	0	0	0	...	0	0
	1	0	0	0	0	1	1	...	1	1
RAM-IV	1	0	0	0	0	0	0	...	0	1
	1	0	0	0	0	1	1	...	1	1

Diagram:

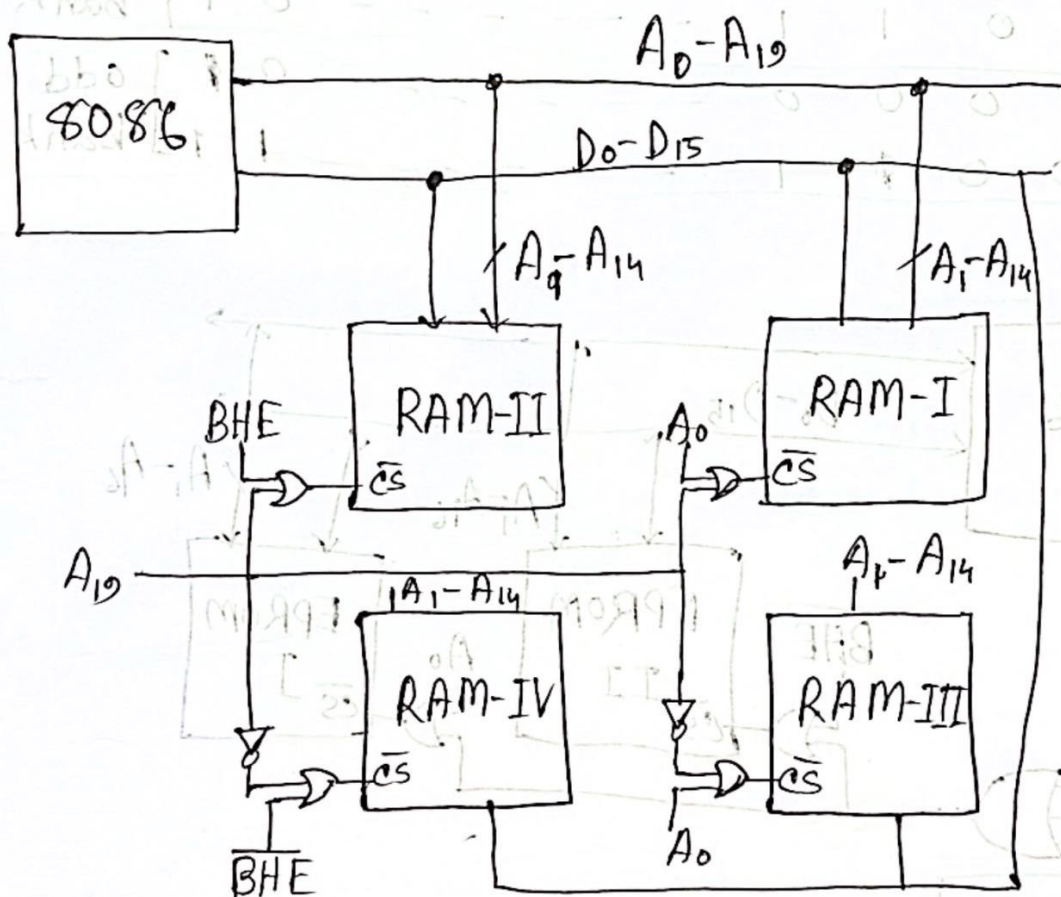

P-4: Interface microprocessor 8086 with two number of IC-27512 chip.

Solⁿ:

Given that,

2 number of IC-27512 $\rightarrow$ EPROM

$$\therefore \text{memory size} = \frac{512}{8} \text{ KB} = 64 \text{ KB}$$


$$= 2^6 \times 8$$

$$\therefore \text{Address line} = 16$$

$$= 2^{16} \times 8$$

	A_{19}	A_{18}	A_{17}	A_{16}	A_{15}	...	A_1	A_0	
EPROM - I	0	0	0	0	0	...	0	0	Even bank
	0	0	0	1	1	...	0	1	
EPROM - II	0	0	0	0	0	...	0	0	odd bank
	0	0	0	1	1	...	1	1	

Diagram

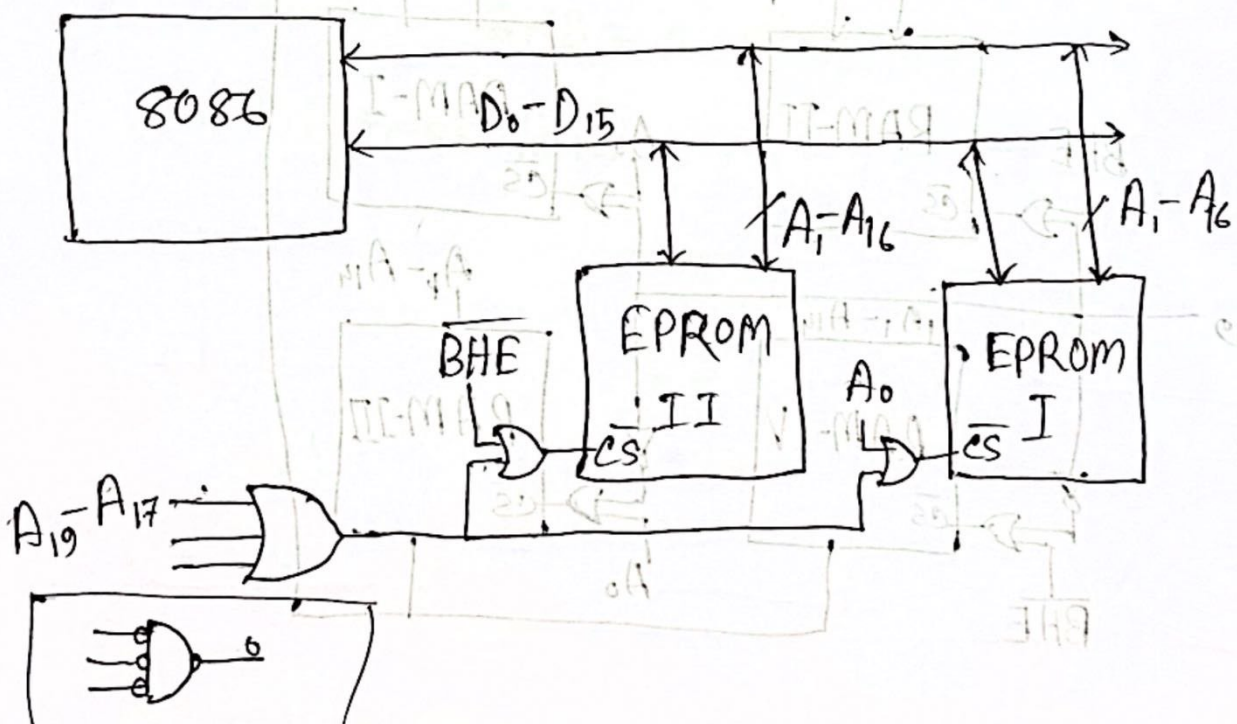

P-5: Interface 16Kx8 memory location for microprocessor 8086. The starting of the microprocessor is C0000H.

Solⁿ: Given that, starting address = C0000H
Total memory location 16Kx8

For even and odd bank = $\frac{16KB}{2} = 8KB$


$$= 2^3 \cdot 2^{10} \times 8$$

$$= 2^{13} \times 8$$

Address line = 13

	A ₁₉	A ₁₈	A ₁₇	A ₁₆	A ₁₅	A ₁₄	A ₁₃	A ₁₂	...	A ₁	A ₀	
Memory I	1	0	0	0	0	0	0	0	...	0	0	Even bank
Memory II	1	0	0	0	0	0	0	0	...	0	1	odd bank

Diagram

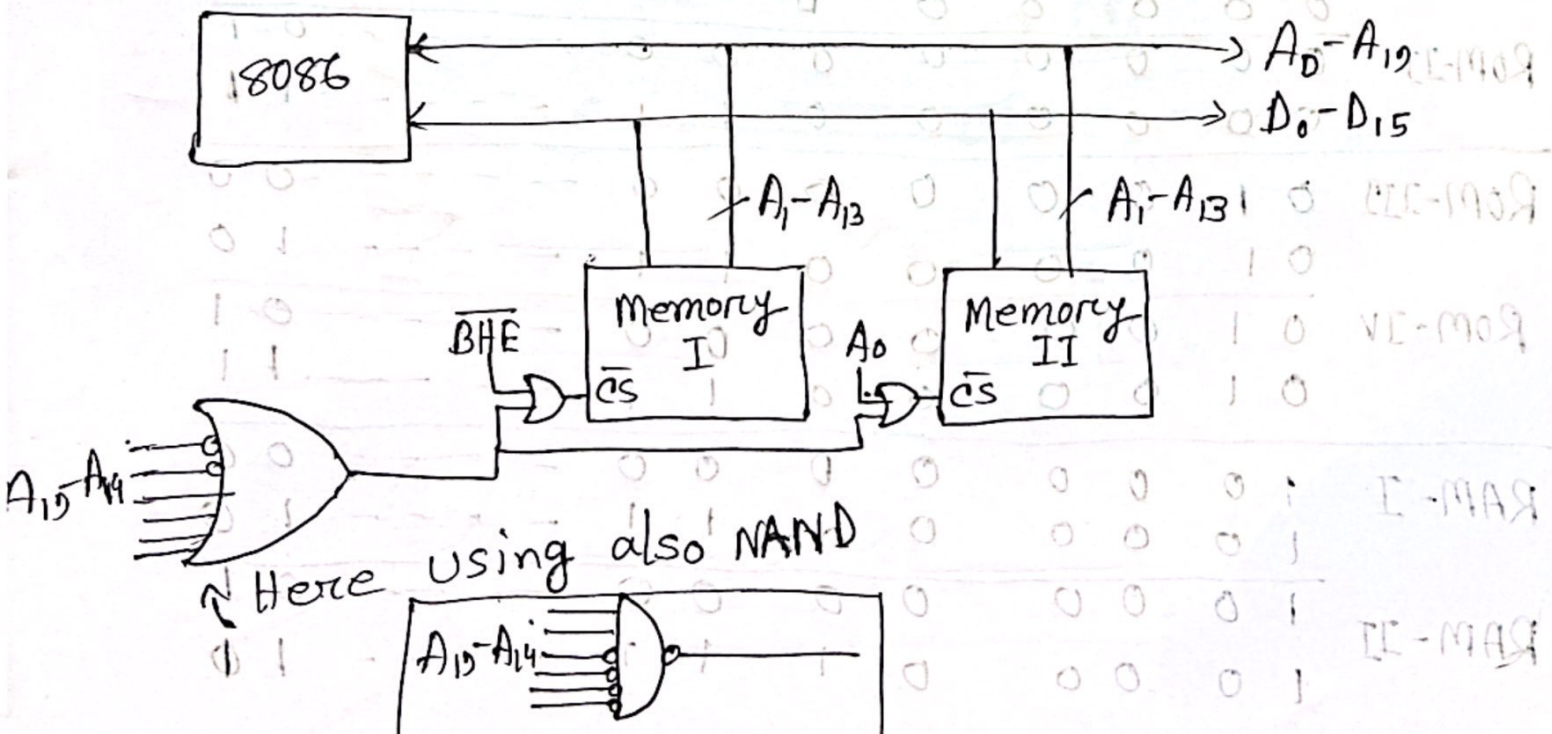

P-6 Interface 32KB ROM using 8KB ROM and 32 KB RAM using 16 KB chips with 8086.

Soln:

Given that,

Total memory 32KB

For ROM:

$$\text{Required no. of ROM} = \frac{32 \text{ KB}}{8 \text{ KB}} = 4$$

$$\text{memory size} = 8 \text{ KB} = 2^3 \cdot 2^{10} \times 8 = 2^{13} \times 8$$

$$AL = 13$$

For RAM:


$$\text{Required no. of RAM} = \frac{32 \text{ KB}}{16 \text{ KB}} = 2$$

$$\text{Memory size} = 16 \text{ KB} = 2^4 \cdot 2^{10} \times 8 = 2^{14} \times 8$$

$$AL = 14$$

	A_{19}	A_{18}	A_{17}	A_{16}	A_{15}	A_{14}	A_{13}	A_{12}	...	...	A_1	A_0
ROM-I	0	0	0	0	0	0	0	0	---	---	0	0
	0	0	0	0	0	0	1	1	---	---	1	0
ROM-II	0	0	0	0	0	0	0	0	---	---	0	1
	0	0	0	0	0	0	1	1	---	---	1	1
ROM-III	0	1	0	0	0	0	0	0	---	---	0	0
	0	1	0	0	0	0	1	1	---	---	1	0
ROM-IV	0	1	0	0	0	0	0	0	---	---	0	1
	0	1	0	0	0	0	1	1	---	---	1	1
RAM-I	1	0	0	0	0	0	0	0	---	---	0	0
	1	0	0	0	0	1	1	1	---	---	1	0
RAM-II	1	0	0	0	0	0	0	0	---	---	0	1
	1	0	0	0	0	1	1	1	---	---	1	1

Diagram :

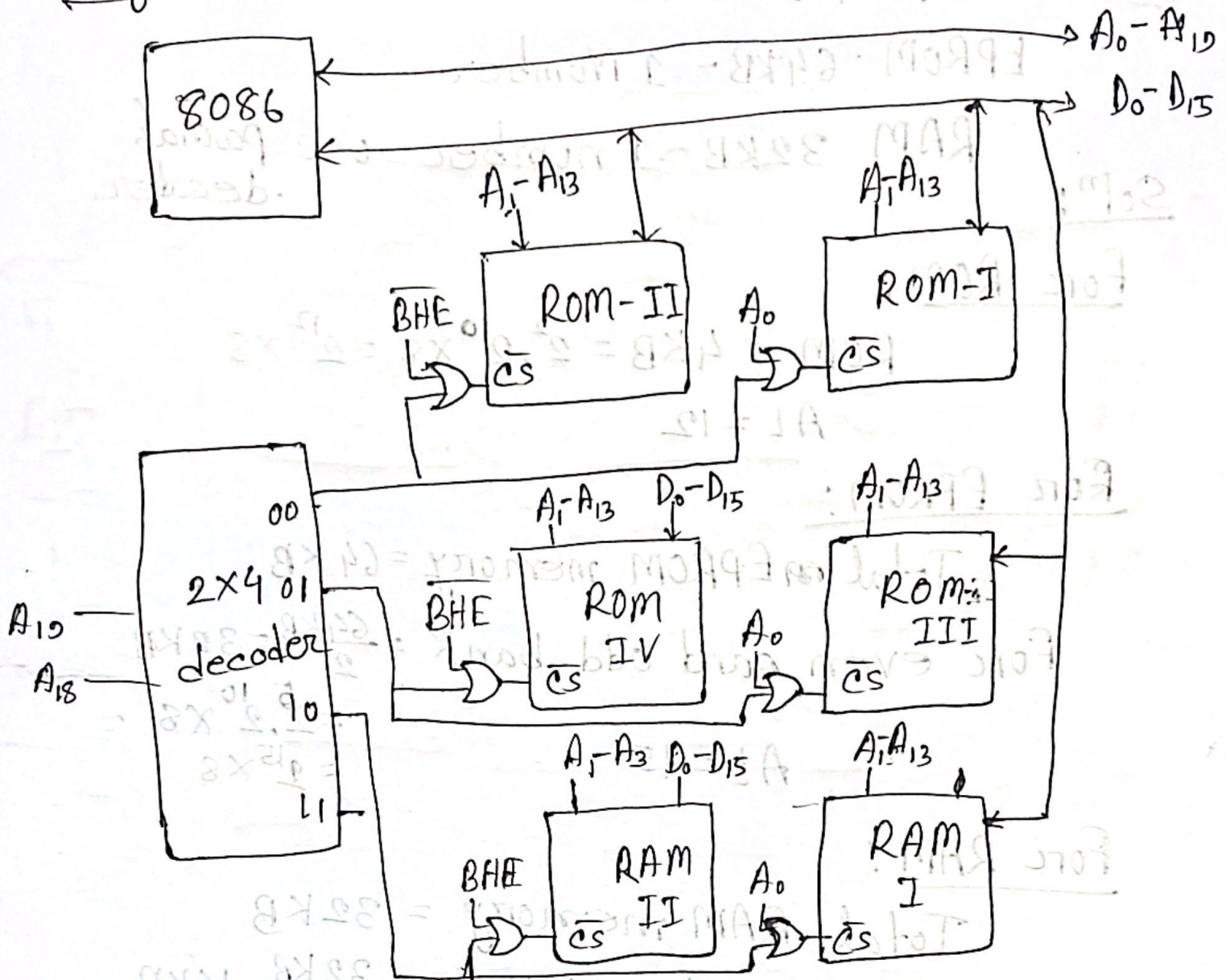

P-71 ROM 4KB - 2 Number

EPROM 64KB - 1 Number

RAM 32KB - 1 number use partial decoder.

Solⁿ:

For ROM:

$$\text{ROM} \rightarrow 4\text{KB} = 2^2 \cdot 2^{10} \times 8 = 2^{12} \times 8$$

$$AL = 12$$

For EPROM:

Total EPROM memory = 64KB

$$\text{For even and odd bank} = \frac{64\text{KB}}{2} = 32\text{KB}$$

$$= 2^5 \cdot 2^{10} \times 8 = 2^{15} \times 8$$

$$AL = 15$$

For RAM:

Total RAM memory = 32KB

$$\text{For even and odd bank} = \frac{32\text{KB}}{2} = 16\text{KB}$$

$$= 2^4 \cdot 2^{10} \times 8 = 2^{14} \times 8$$

$$AL = 14$$

	A_{19}	A_{18}	A_{17}	A_{16}	A_{15}	A_{14}	A_{13}	A_{12}	A_{11}	...	A_1	A_0
ROM-I	0	0	0	0	0	0	0	0	0	...	0	0
	0	0	0	0	0	0	0	1	1	...	1	0
ROM-II	0	0	0	0	0	0	0	0	0	...	0	1
	0	0	0	0	0	0	0	1	1	...	1	1
EPROM I	0	1	0	0	0	0	0	0	0	...	0	0
	0	1	0	0	1	1	1	1	1	...	1	0
EPROM II	0	1	0	0	0	0	0	0	0	...	0	1
	0	1	0	0	1	1	1	1	1	...	1	1
RAM-I	1	0	0	0	0	0	0	0	0	...	0	0
	1	0	0	0	0	1	1	1	1	...	1	0
	1	0	0	0	0	0	0	0	0	...	0	1
	1	0	0	0	0	1	1	1	1	...	1	1

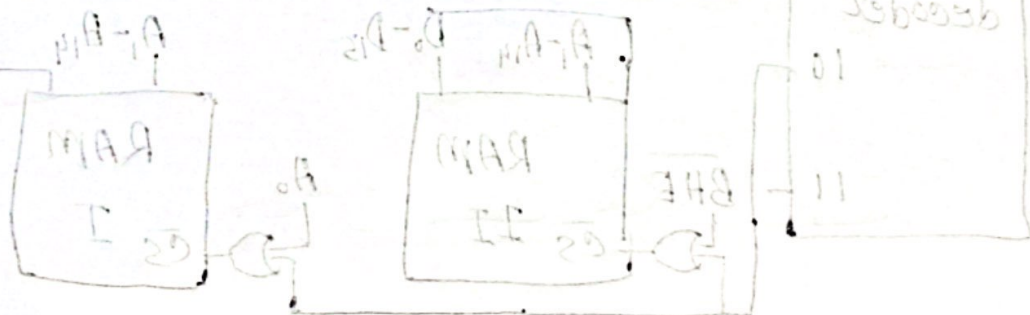


Diagram:

